

Computer Architecture (CSC-3501) Lecture 4 (24 Jan 2008)

Seung-Jong Park (Jay)
<http://www.csc.lsu.edu/~sjpark>

1

CSC3501 – S.J. Park

Announcement

- 1st Homework's due date is tomorrow
 - Due date will be 72 hours later

2


Objectives of Ch. 4

- Understand the relationship between Boolean logic and digital computer circuits.
- Learn how to design simple logic circuits.
- Understand how digital circuits work together to form complex computer systems

3


Why do we need to learn logic ?

- *“The Intel Core 2 Duo desktop processor is an energy-efficient marvel, packing 291 million transistors yet consuming lower power”*
from Intel
- We need to know relationships between transistors and computers
 - Transistors comprise basic logic gates, e.g., AND, OR, NOT, NAND, NOR, XOR, etc.
 - Basic logic gates comprise complicated functional units, e.g., adder, counter, memory, CPU
 - Finally, computer is built with those complicated functional units

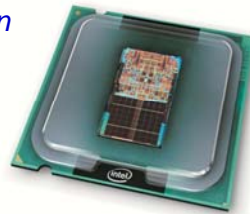

4

Computer Architecture

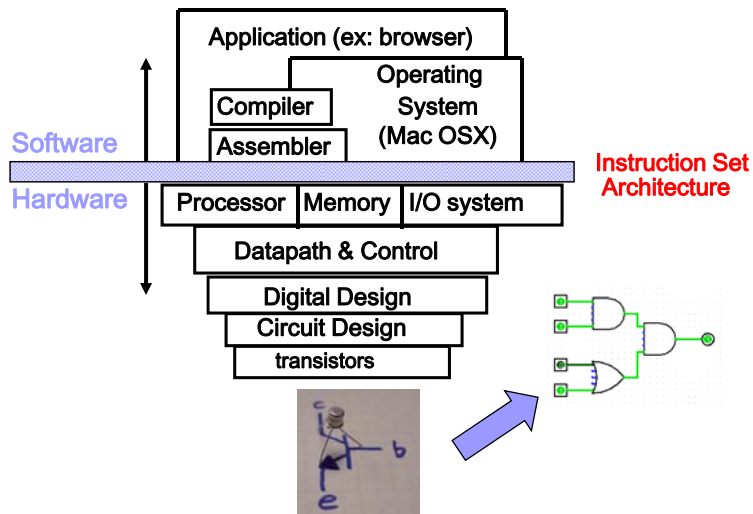


5

Basic Logic Gates


- Perform logic functions:
 - Inversion (NOT), AND, OR, NAND, NOR, etc.
- Single-input:
 - NOT gate, buffer
- Two-input:
 - AND, OR, XOR, NAND, NOR, XNOR
- Multiple-input

Single-Input Logic Gates

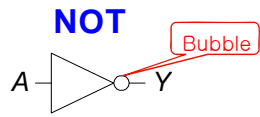

$$Y = \bar{A}$$


A	Y
0	1
1	0

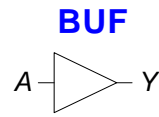

$$Y = A$$


A	Y
0	0
1	1

Two-Input Logic Gates

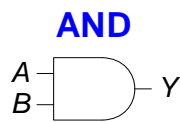

$$Y = AB$$





A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

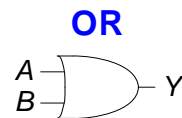

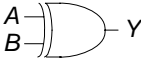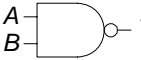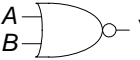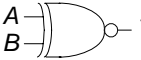
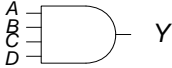
$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1



More Two-Input Logic Gates

XOR	NAND	NOR	XNOR																																																												
																																																															
$Y = A \oplus B$	$Y = \overline{AB}$	$Y = \overline{A + B}$	$Y = \overline{A \oplus B}$																																																												
<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1
A	B	Y																																																													
0	0	0																																																													
0	1	1																																																													
1	0	1																																																													
1	1	0																																																													
A	B	Y																																																													
0	0	1																																																													
0	1	1																																																													
1	0	1																																																													
1	1	0																																																													
A	B	Y																																																													
0	0	1																																																													
0	1	0																																																													
1	0	0																																																													
1	1	0																																																													
A	B	Y																																																													
0	0	0																																																													
0	1	0																																																													
1	0	0																																																													
1	1	1																																																													

Multiple-Input Logic Gates



NOR3	AND4																																				
																																					
$Y = \overline{A+B+C}$	$Y = ABCD$																																				
<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr><th>A</th><th>B</th><th>C</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	C	Y	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1		
A	B	C	Y																																		
0	0	0																																			
0	0	1																																			
0	1	0																																			
0	1	1																																			
1	0	0																																			
1	0	1																																			
1	1	0																																			
1	1	1																																			

Transistor

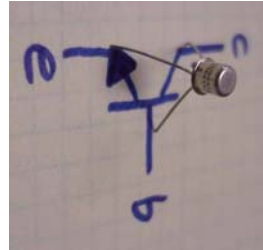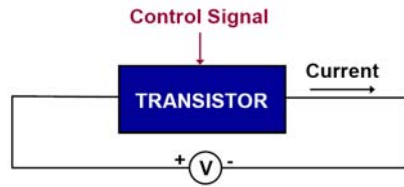

Switch (Digital Electronics)

Amplifier (Analog Electronics)

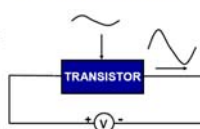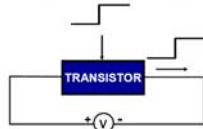


E.g., Microprocessor, Memory

E.g., Sensor, Radio

Transistor

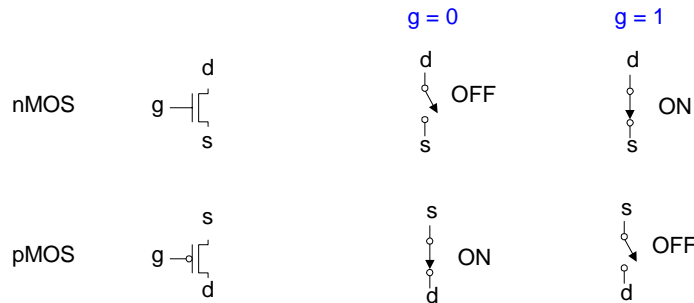
- Transistor is a three-ported voltage-controlled switch
 - Two of the ports (drain and source) are connected depending on the voltage on the third port (gate)
 - For example, in the switch below the two terminals (d and s) are connected (ON) only when the third terminal (g) is 1



Different Kinds of Transistors


■ Junction Transistor

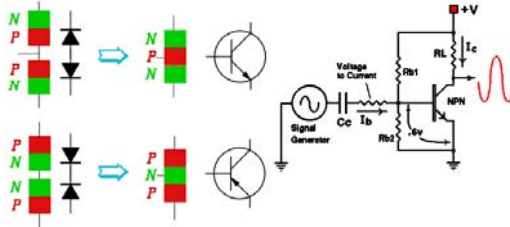- A Bipolar Transistor essentially consists of a pair of PN Junction Diodes that are joined back-to-back.
- It acts as an amplifier or a switch




■ Metal oxide silicon (MOS) transistors

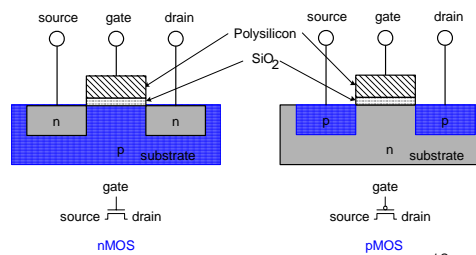- Polysilicon (used to be **metal**) gate
- **Oxide** (silicon dioxide) insulator
- Doped **silicon** substrate and wells




How to Build Basic Logic Gates

■ Build NOT gate with transistors

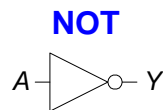

$$Y = \overline{A}$$

A	Y
0	1
1	0

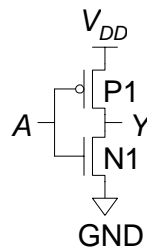


A	P1	N1	Y
0	ON	OFF	1
1	OFF	ON	0

How to build Basic Logic Gates


- Build a NAND gate with transistors

NAND

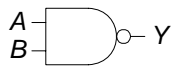

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

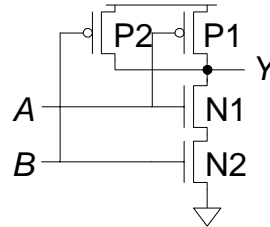


A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0


15

How to Build Other Logic Gates

- Build a AND gate with NAND gate

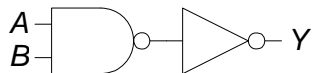

- Build a OR gate with NAND gate

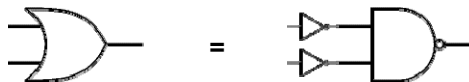

- Therefore, NAND gate is a basic unit to build complicated functional logic circuits
- NOW!**, we know that transistors are fundamental components to build a computer !!!

16

Boolean Algebra

- Boolean algebra is a mathematical system for the manipulation of variables that can have one of two values.
 - In formal logic, these values are “true” and “false.”
 - In digital systems, these values are “on” and “off,” 1 and 0, or “high” and “low.”
- Boolean expressions are created by performing operations on Boolean variables.
 - Common Boolean operators include AND, OR, and NOT.

17

Boolean Algebra

- A Boolean operator can be completely described using a truth table.
- The truth table for the Boolean operators AND and OR are shown at the right.
- The AND operator is also known as a Boolean product. The OR operator is the Boolean sum.
- The truth table for the Boolean NOT operator is shown at the right.
- The NOT operation is most often designated by an overbar. It is sometimes indicated by a prime mark (') or an “elbow” (\neg).

X AND Y		
X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT X	
X	\bar{X}
0	1
1	0

18

Boolean Function

- A Boolean function has:
 - At least one Boolean variable,
 - At least one Boolean operator, and
 - At least one input from the set $\{0,1\}$.
- It produces an output that is also a member of the set $\{0,1\}$.

Now you know why the binary numbering system is so handy in digital systems.

19

Boolean Function

- The truth table for the Boolean function:

$$F(x, y, z) = x\bar{z} + y$$

is shown at the right.

- To make evaluation of the Boolean function easier, the truth table contains extra (shaded) columns to hold evaluations of subparts of the function

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

20

Boolean Function

- As with common arithmetic, Boolean operations have rules of precedence.
- The NOT operator has highest priority, followed by AND and then OR.
- This is how we chose the (shaded) function subparts in our table.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

To be continued ...more complicated Boolean Algebra.