



# Computer Architecture (CSC-3501) Lecture 6 (31 Jan 2008)

Seung-Jong Park (Jay)  
<http://www.csc.lsu.edu/~sjpark>

1



CSC3501 – S.J. Park


## Announcement

2
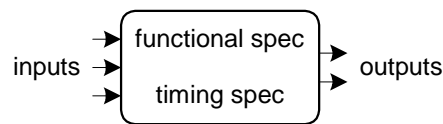
## Reminder

A logic circuit is composed of:

- Inputs
- Outputs
- Functional specification
- Timing specification



## Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row in a truth table has a minterm
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- The function is formed by ORing the minterms for which the output is TRUE
- Thus, a sum (OR) of products (AND terms)

$$Y = F(A, B, C) = \overline{A}B + A\overline{B}$$

| A | B | Y | minterm                     |
|---|---|---|-----------------------------|
| 0 | 0 | 0 | $\overline{A} \overline{B}$ |
| 0 | 1 | 1 | $\overline{A} B$            |
| 1 | 0 | 0 | $A \overline{B}$            |
| 1 | 1 | 1 | $A B$                       |

## Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row in a truth table has a maxterm
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- The function is formed by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)


$$Y = F(A, B, C) = (A + B)(A + B)$$

| A | B | Y | maxterm             |
|---|---|---|---------------------|
| 0 | 0 | 0 | $A + B$             |
| 0 | 1 | 1 | $A + \bar{B}$       |
| 1 | 0 | 0 | $\bar{A} + B$       |
| 1 | 1 | 1 | $\bar{A} + \bar{B}$ |

5

 
## Circuit Schematic Rules

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection



 
# Bubble Pushing

- Think DeMorgan's law
- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.





 
- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.



2-&lt;7&gt;
   
# NANDs are special!


- The NAND gate is **universal**: it can replace all other gates!



8
 
## Making NAND circuits


- The easiest way to make a NAND circuit is to start with a regular, primitive gate-based diagram.
- Two-level circuits are trivial to convert, so here is a slightly more complex random example.



9
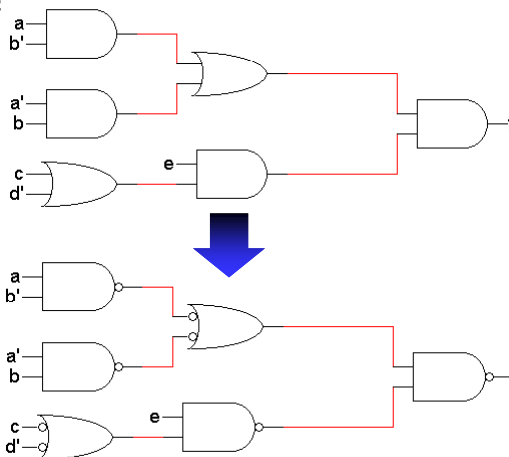
## Converting to a NAND circuit


- Step 1: Convert all AND gates to NAND gates using AND-NOT symbols, and convert all OR gates to NAND gates using NOT-OR symbol



10
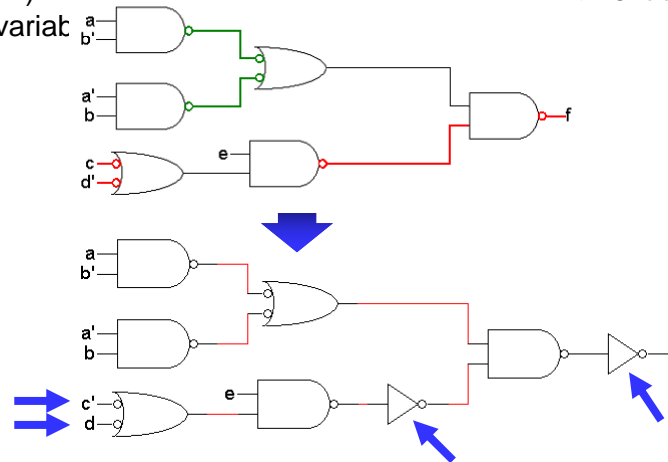
## Converting to NAND, concluded


- **Step 2:** Make sure you added bubbles along lines *in pairs* ( $((x')') = x$ ). If not, then either add inverters or complement the input variat



11
 
## Combinational vs. Sequential Logic


- **Combinational Logic**
  - Memoryless
  - Outputs determined by current values of inputs
- **Sequential Logic**
  - Has memory
  - Outputs determined by previous and current values of inputs
- **Reference**
  - "Logic and Computer Design Fundamentals" by Mano  
<http://www.writphotec.com/mano/>



12
 
## Combinational Logic

- Every circuit element is itself combinational
- Every node of the circuit is either designated as an input to the circuit or connects to exactly one output terminal of a circuit element
- The circuit contains no cyclic paths: every path through the circuit visits each circuit node at most once
- Example:



13

## Basic Combinational Logics


- Arithmetic Functions
  - ADD, Subtract, Multiply, Division
- Encoder/Decoder
- Multiplexer(Selector) /Demultiplexer

14

# Half Adder

- Combinational logic
- One of the simplest is the *half adder*, which finds the sum of two bits.
- We can gain some insight as to the construction of a half adder by looking at its truth table, shown at the right.
- As we see, the sum can be found using the XOR operation and the carry using the AND operation.

| Inputs |   | Outputs |       |
|--------|---|---------|-------|
| X      | Y | Sum     | Carry |
| 0      | 0 | 0       | 0     |
| 0      | 1 | 1       | 0     |
| 1      | 0 | 1       | 0     |
| 1      | 1 | 0       | 1     |

 


15

# Full Adder

- We can change our half adder into a full adder by **including gates for processing the carry bit**.
- The truth table for a full adder is shown at the right.

| Inputs |   |          | Outputs |           |
|--------|---|----------|---------|-----------|
| X      | Y | Carry In | Sum     | Carry Out |
| 0      | 0 | 0        | 0       | 0         |
| 0      | 0 | 1        | 1       | 0         |
| 0      | 1 | 0        | 1       | 0         |
| 0      | 1 | 1        | 0       | 1         |
| 1      | 0 | 0        | 1       | 0         |
| 1      | 0 | 1        | 0       | 1         |
| 1      | 1 | 0        | 0       | 1         |
| 1      | 1 | 1        | 1       | 1         |

 


16


 
# Ripple Carry Adder

- Just as we combined half adders to make a full adder, full adders can be connected in series.
- The carry bit “ripples” from one adder to the next; hence, this configuration is called a *ripple-carry adder*.




- **Today's systems employ more efficient adders.**
  - Carry look-ahead adder

17
 
# Enable

- *Enable* is a common input to logic functions
  - See it in memories, and today's blocks
  - *Change value inside buffer or memory*



18

# Decoder

- Decoders are another important type of combinational circuit.
- Among other things, they are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.
- Address decoders with  $n$  inputs can select any of  $2^n$  locations.





19

# 2-to-4 Decoder

- Truth table for 2-to-4 decoder ?

| x | y | $xy$ | $\bar{x}\bar{y}$ | $\bar{x}y$ | $x\bar{y}$ |
|---|---|------|------------------|------------|------------|
| 0 | 0 |      |                  |            |            |
| 0 | 1 |      |                  |            |            |
| 1 | 0 |      |                  |            |            |
| 1 | 1 |      |                  |            |            |

  

20

## 3-to-8 Decoder

| Inputs         |                |                | Outputs        |                |                |                |                |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A <sub>2</sub> | A <sub>1</sub> | A <sub>0</sub> | D <sub>7</sub> | D <sub>6</sub> | D <sub>5</sub> | D <sub>4</sub> | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> |
| 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              |
| 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              |
| 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 0              | 1              | 1              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 1              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              |
| 1              | 0              | 1              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              |
| 1              | 1              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              |
| 1              | 1              | 1              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |

- Notice that outputs are **minterms**

21

## Encoder

- Encoder is the opposite of decoder
- 2<sup>n</sup> inputs
- n outputs

22

## Truth Table of 8-to-3 Encoder

| Inputs         |                |                |                |                |                |                |                | Outputs        |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D <sub>7</sub> | D <sub>6</sub> | D <sub>5</sub> | D <sub>4</sub> | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> | A <sub>2</sub> | A <sub>1</sub> | A <sub>0</sub> |
| 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              |
| 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
| 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 1              |
| 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 1              |
| 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 0              |
| 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 1              |

23

## Inputs are Minterms

- Can OR them together appropriately
- $A_0 = D_1 + D_3 + D_5 + D_7$

| Inputs         |                |                |                |                |                |                |                | Outputs        |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D <sub>7</sub> | D <sub>6</sub> | D <sub>5</sub> | D <sub>4</sub> | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> | A <sub>2</sub> | A <sub>1</sub> | A <sub>0</sub> |
| 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              |
| 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
| 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 1              |
| 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 1              |
| 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 0              |
| 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 1              |

24

## What's the Problem?

- What if D3 and D6 both high?

| Inputs         |                |                |                |                |                |                |                | Outputs        |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D <sub>7</sub> | D <sub>6</sub> | D <sub>5</sub> | D <sub>4</sub> | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> | A <sub>2</sub> | A <sub>1</sub> | A <sub>0</sub> |
| 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              |
| 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
| 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 1              |
| 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 1              |
| 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 0              |
| 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 1              |

25

## Priority Encoder

- Chooses one with highest priority
  - Largest number, usually
- Note "don't cares"

| Inputs         |                |                |                | Outputs        |                |
|----------------|----------------|----------------|----------------|----------------|----------------|
| D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> | A <sub>1</sub> | A <sub>0</sub> |
| 0              | 0              | 0              | 1              | 0              | 0              |
| 0              | 0              | 1              | X              | 0              | 1              |
| 0              | 1              | X              | X              | 1              | 0              |
| 1              | X              | X              | X              | 1              | 1              |

**What if all inputs are zero?**

26

## Need Another Output

| Inputs         |                |                |                | Outputs        |                |   |
|----------------|----------------|----------------|----------------|----------------|----------------|---|
| D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> | A <sub>1</sub> | A <sub>0</sub> | V |
| 0              | 0              | 0              | 0              | X              | X              | 0 |
| 0              | 0              | 0              | 1              | 0              | 0              | 1 |
| 0              | 0              | 1              | X              | 0              | 1              | 1 |
| 0              | 1              | X              | X              | 1              | 0              | 1 |
| 1              | X              | X              | X              | 1              | 1              | 1 |

27

## Valid is OR of inputs


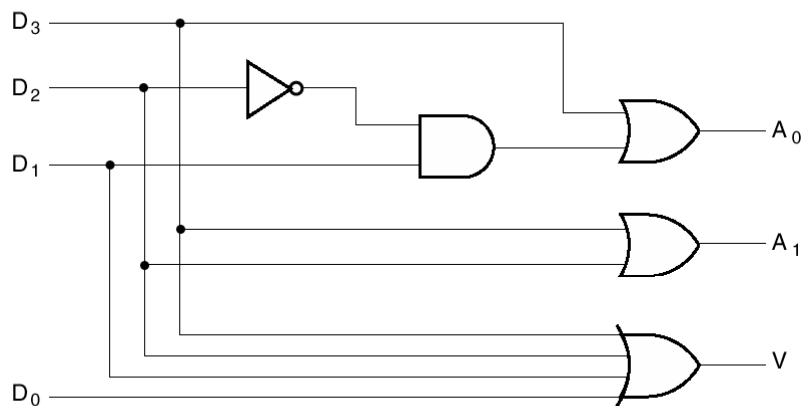
 


Fig. 3-18 Logic Diagram of a 4-Input Priority Encoder

28
 
# Multiplexer

- A multiplexer does just the opposite of a decoder.
- It selects a single output from several inputs.
- The particular input chosen for output is determined by the value of the multiplexer's control lines.
- To be able to select among  $n$  inputs,  $\log_2 n$  control lines are needed.




If  $S_0 = 1$  and  $S_1 = 0$ , which input is transferred to the output?

29
 
# Combinational vs. Sequential ?

- Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.
- There are other times, however, when we need a circuit to change its value with consideration to its current state as well as its inputs.
  - These circuits have to “remember” their current state.
- *Sequential logic circuits* provide this functionality for us.
- **Example:** design vending machine which sells something for 4 coins
  - Vending machine A with 4 input holes
  - Vending machine B with 1 input hole



30